



Buck Converter Design Project

EE365 - Power Electronics

Supervisor: Prof. Drazen Dujic

Assistants: Miodrag Basić, Nikolina Djekanović, Xiaotong Du,
Nicolai Hildebrandt, Milan Utvić

Project Designers - Group 1:

Pierre Tarazi 288217

Teng Kuan Hsieh 320027

❑ Goal of project:

- ❑ Design a Buck converter with the following specifications.

❑ Specification:

- ❑ $32 \text{ V} \leq V_{\text{in}} \leq 48 \text{ V}.$
- ❑ $V_{\text{out}} = 24 \text{ V}.$
- ❑ $f_{\text{switch}} = 50 \text{ kHz}.$
- ❑ $P_{\text{Nominal}} = 50 \text{ W}.$
- ❑ $I_{\text{L, peak ripple}} = 10\% \cdot I_{\text{L}}$
- ❑ $V_{\text{out, peak ripple}} = 1\% \cdot V_{\text{out}}$


1. Buck Converter Specifications

- I/O Voltage transfer function:
 $V_{out}/V_{in} = D$ (range: 0.5 - 0.75)
 $\Delta I_L = \frac{V_{out}}{L_{min}} (1 - D) T_s$
 $L_{min} = L_{selected} = 1.2 \text{ mH}$ ($D = 0.5$)
 $C_{min} = \frac{\Delta I_L T_s}{8 \Delta V_{out}} = 2.167 \text{ }\mu\text{F}$,
 $C_{selected} = 2.2 \text{ }\mu\text{F}$


2. Semiconductor Components

- $I_{L,Max} = I_L + \frac{\Delta I_{L,pp}}{2}$
 $= I_{MOSFET,max} = I_{diode,max} = 2.184 \text{ A}$
- $V_{MOSFET,max} = V_{diode,max} = 48 \text{ V}$
- MOSFET model 4: ZXMN10A11K
- Diode model 1: B3100-13-F

PLECS verification through simulations

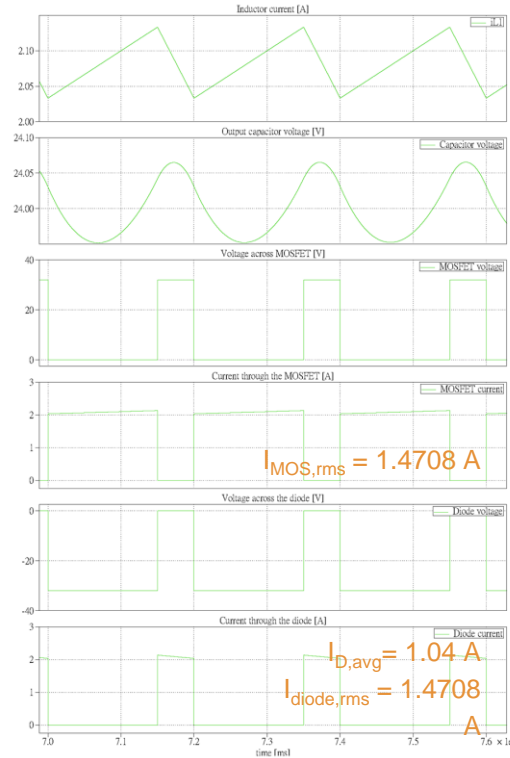

$V_{in} = 48 \text{ V}$ with $D = 0.75$

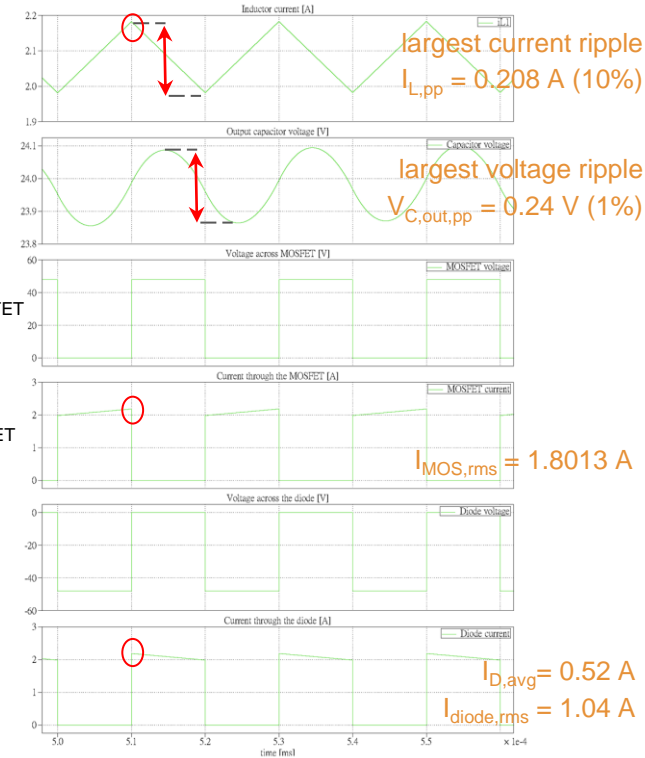

$V_{in} = 32 \text{ V}$ with $D = 0.5$

3. Buck Converter Power Losses



- ❑ Choice of the operating point: $V_{in} = 32 \text{ V}$, $P_{out} = 50 \text{ W}$.
- ❑ $P_{cond,MOS} = R_{DS,on} \cdot I_{D,rms}^2 = 0.6 \times 1.82^2$
- ❑ $P_{cond,Diode} = U_{D0} \cdot I_{D,avg} + R_D \cdot I_{D,rms}^2 = 0.2 \times 0.525 + 0.2 \times 1.05^2$
- ❑ $P_{on,MOS} = E_{on,MOS} \cdot f_{sw}$
 - ❑ $E_{on,MOS} \cong V_{in} \cdot I_L \cdot (t_{ri} + t_{fu}) / 2$
- ❑ $P_{off,MOS} = E_{off,MOS} \cdot f_{sw}$
 - ❑ $E_{off,MOS} \cong V_{in} \cdot I_{d,off} \cdot (t_{ru} + t_{fi}) / 2$ with $I_{d,off} = I_{L,max} = 2.184 \text{ A}$
- ❑ MATLAB losses tool verification

Property	Value	Unit
L	1.2	mH
C	2.2	μF
$P_{cond,MOSFET}$	1.99	W
$P_{on,MOSFET}$	7.6	mW
$P_{off,MOSFET}$	14.9	mW
$P_{cond,DIODE}$	0.33	W
P_{total}	2.3425	W
Efficiency	95.31	%
MOSFET model	4	
DIODE model	1	

$P_{sw,MOS} = 22.5 \text{ mW}$

$$P_{ttl} = P_{cond,M} + P_{cond,D} + P_{on,M} + P_{off,M}$$
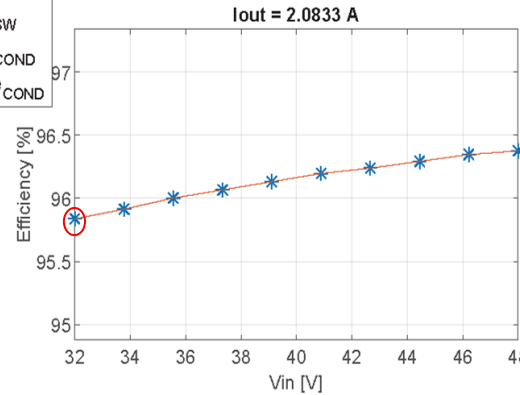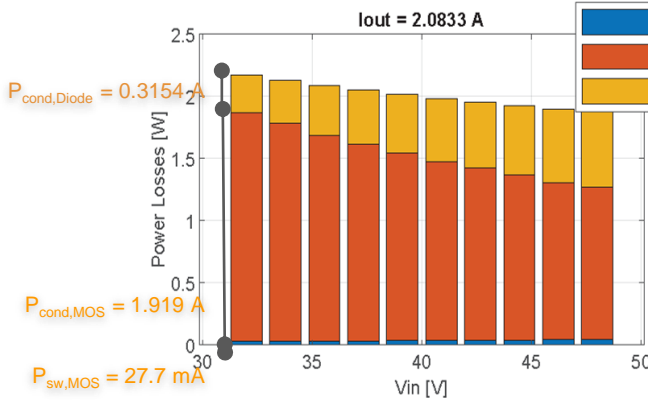
$$\eta = \frac{P_{out} - P_{ttl}}{P_{in}}$$



- ❑ Heatsink selection for diode and MOSFET

12V, 2W
($P_{aux,min} \cong 0.245 \text{ W}$)

Verify the theoretical ESR ($\Delta V_{C,out,ripple} / \Delta I_{L,ripple}$) with the value from data sheet of C_{out} model

3. Auxiliary Power Supply

1. Inductor I/O components

$$C_{DRV} = 10 \cdot C_{BST} = 0.68 \mu\text{F}$$


1. Select R_{in} , C_{in} , R_{out} , C_{out}

Power dissipations: P_{ESR} , $P_{R,in}$, $P_{R,out}$

2. Select R_{shunt} , R_f , C_f

Power dissipation: P_{shunt}

Bode Diagram

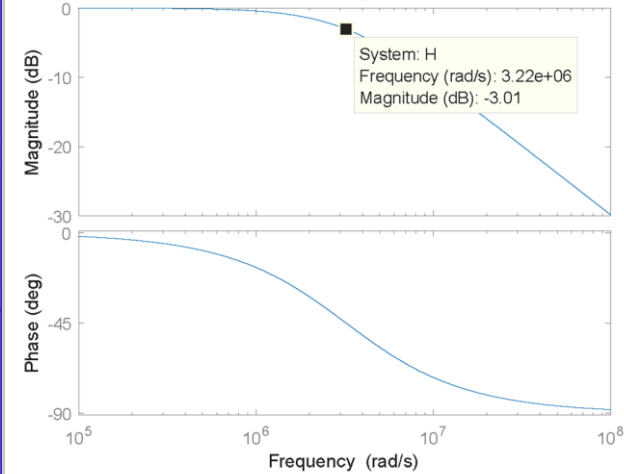

2. Current Measurement IC


Current measurement filtering: R_f & C_f for the desired cutoff frequency ($f_c = 1/(4\pi RC) = 500 \text{ kHz}$)

Current Measurement Filtering


5. Half Bridge Gate Driver



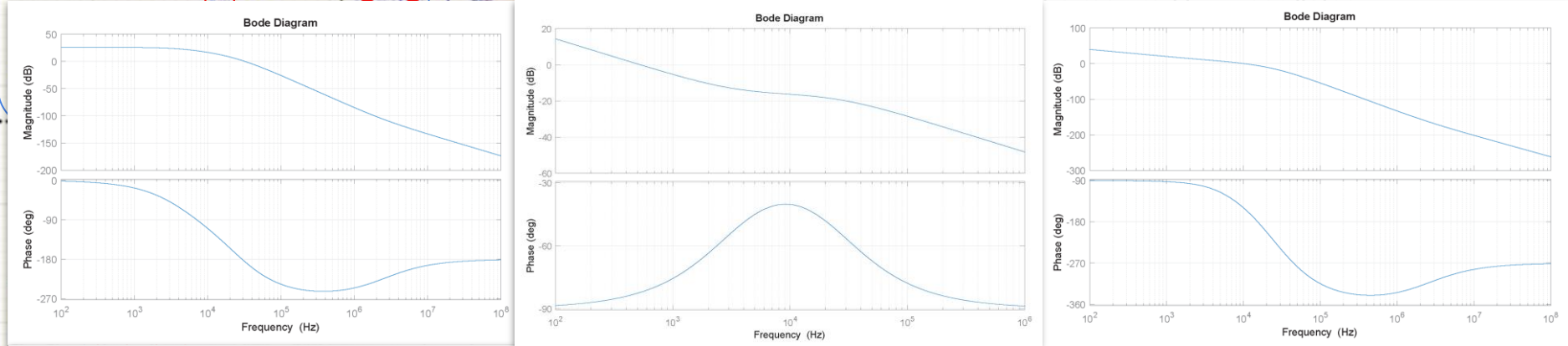4. $C_{\text{soft start}}$ for 10 ms start-up time ($t_{\text{ss}} = 9 \times 10^4 \cdot C_{\text{ss}}$);
 R_1, R_2, R_3 for under-and-over-voltage protection;



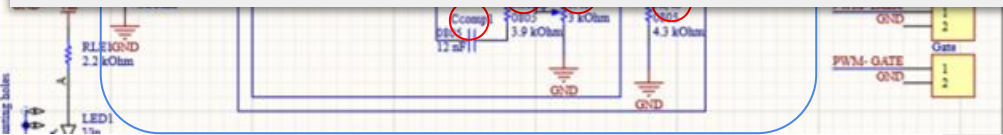
Transfer functions:
Left: Control-to-Output; Center: Compensator; Right: Final Control-to-Output with Compensator




Bootstrap, start-up & zener diodes

4. PWM Controller IC

PCB schematic

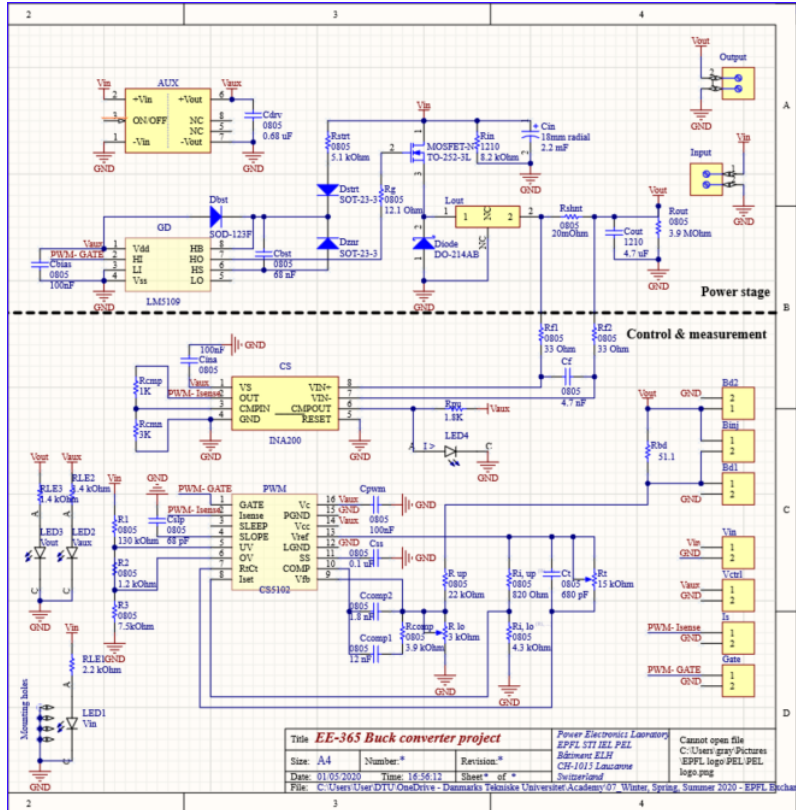

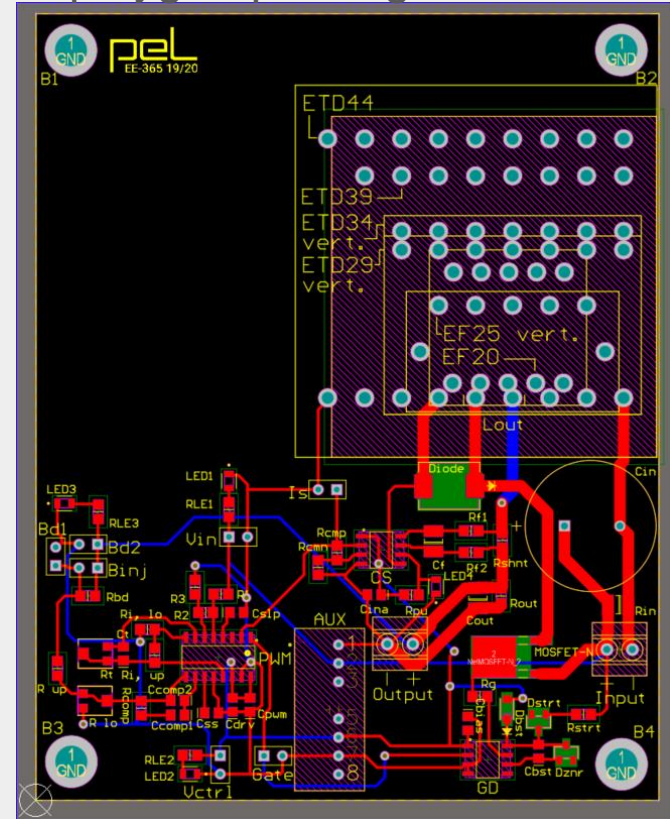
PCB layout overview with polygon pourings shelved



1. Inductor specification & Design constraints


- $B_{\max} = 0.3 \text{ T}$
- $K_u = 0.5$
- $R_{L,\max} = 0.22 \Omega$ (2% P_{out})
- $J_W = 2 \text{ A/mm}^2$

2. Preselection of inductor cores

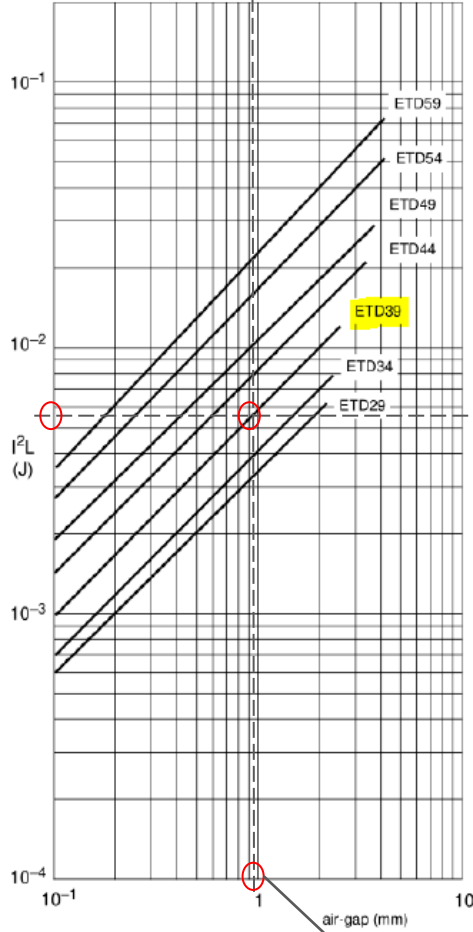


I²L chart

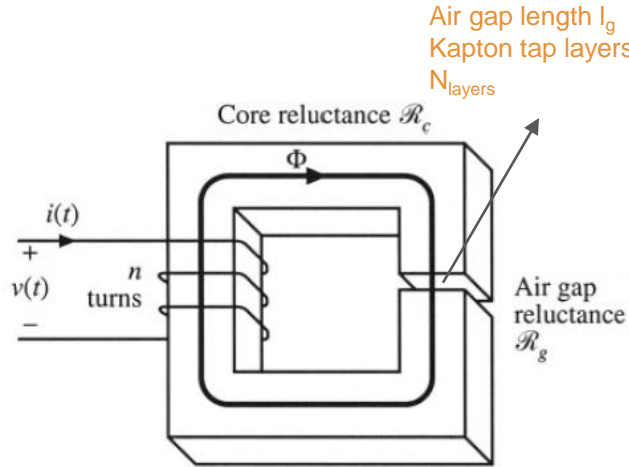$l_{g,\text{estimate}} = 0.95 \text{ mm}$



Inductor Geometry

Inductor Core model: ETD39/20/13

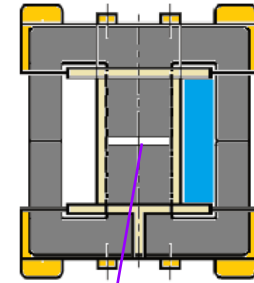


Core c-s area A_c

$$A_{p,\text{core}} = W_{A,\text{eff}} \cdot A_c$$


$$\geq A_{p,\text{min}} = (L \cdot I_{L,\text{pk}} \cdot I_{L,\text{rms}}) / (B_{\max} \cdot J_W \cdot K_u)$$

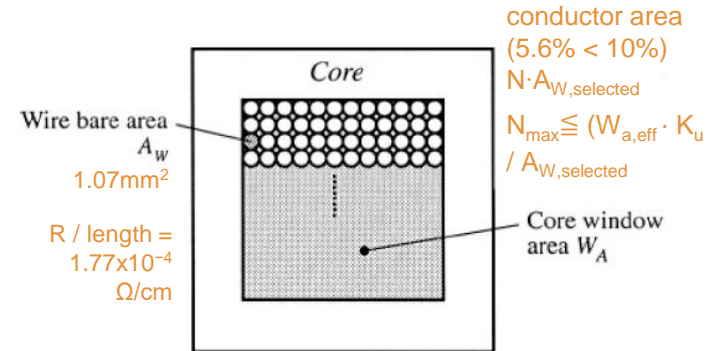3. Magnetic wire selection & number of turns calculation



Core Window Area Utilization

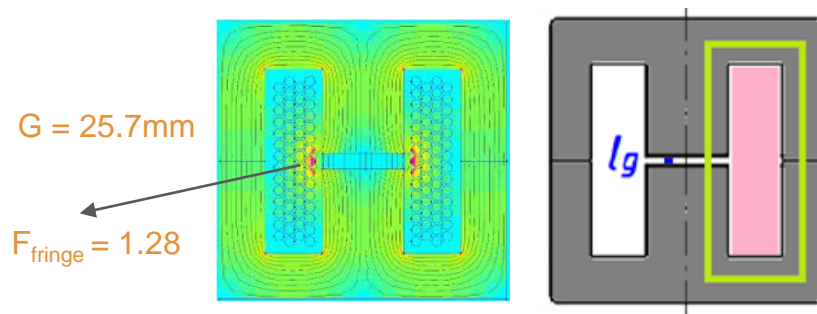4. Calculation of air gap length, fringing flux factor & adjustment of N_{selected} with F_{fringe}



Fringing flux induced copper losses

$$l_g = (\mu_0 \cdot N_{\text{selected}}^2 \cdot A_C) / L - MPL / \mu_r$$

$$= 0.75 \text{ mm}$$

$$l_{g,\text{estimate}} = 0.95 \text{ mm}$$

$$N_{\text{layers}} = l_g / \text{thickness} \cdot \frac{1}{2} = 5.8$$

thus count 6 layers.

$$N_{\text{new selected}} = \sqrt{\left(l_g + \frac{MPL}{\mu_r} \right) \frac{L/F_{\text{fringe}}}{\mu_0 \cdot A_C}}$$

$$= 68.92$$

5. Verification of the design constraints


$$R_L = N_{\text{new}} \cdot MLT \cdot \frac{R}{\text{length}} = 83 \text{ m}\Omega, \text{ while } R_{L,\text{max}} = 220 \text{ m}\Omega$$

$$P_{\text{Cu,dc}} = 0.38 \text{ W} = 0.76\% P_{\text{out}}$$

$$B_{\text{ac}} = 14.4 \text{ mT}$$

$$B_{\text{pk}} = 302.5 \text{ mT}$$
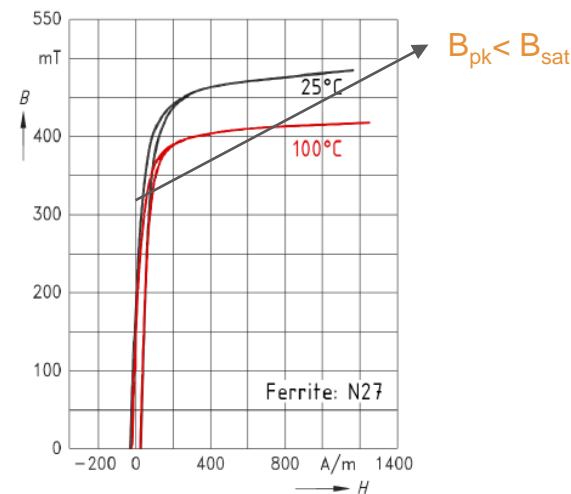
$$K_u = 0.43 \text{ with } N_{\text{new}}$$



Saturation flux density of ferrite N27

❑ Compute the overall efficiency of your Buck converter for the nominal output power.

❑ $\eta_{\text{Buck,best}} = 94.4\%$

with $V_{\text{in}} = 48 \text{ V}$, $P_{\text{loss,R1,min}} = 1.8 \text{ W}$

❑ $\eta_{\text{Buck,worst}} = 93.8\%$

with $V_{\text{in}} = 32 \text{ V}$, $P_{\text{loss,R1,max}} = 2.17 \text{ W}$

Summary table for the Buck Converter Design

Electrical specification

Nominal inductance	L_{nom}	1.2 mH
Effective current	$I_{\text{L,rms}}$	2.14 A
Current ripple	$\Delta I_{\text{L,pk-pk}}$	2.08 A
Ripple frequency	f_{sw}	50 kHz

Core specification

Core shape and size		ETD39/20/13
Coil former		B66364B1016T001
Core material		N27
Peak flux density	B_{pk}	302.5 mT
Air gap length	l_{g}	0.75 mm
Number of Kapton tape layers		6

Winding specification

wire diameter	\varnothing	1.2 mm
number of turns	N	68

Losses and temperature rise

Core losses	P_{core}	0.069 W
Winding losses	$P_{\text{Cu,dc}}$	0.38 W
Total inductor losses	$P_{\text{L,loss}}/P_{\text{out}}$	0.9 %
Temperature rise	ΔT	7.2 K

☐ Challenges/ Problems

- ☐ Understanding how to find the good components on DigiKey
- ☐ Understanding the relationship between the ICs in Report 2 and finding the needed info in the datasheets and Application Notes.

☐ Learnings

- ☐ Extract needed information from application notes and data sheets.
- ☐ How to select a component from DigiKey.
- ☐ How is Buck converter constituted from A to Z.

☐ Feedback for the design project

- ☐ Include more theory related to the project in the lectures.

Cover	Goal & Spec.	R1 - Buck Converter Basic Design	R2 - Schematic & PCB Design	R3 - Inductor Design	Summary & Conclusion	End Cover
-------	--------------	----------------------------------	-----------------------------	----------------------	----------------------	--------------

Thank you for your attention!